



Lab 6

61C Summer 2023




Useful Logisim Components

Splitters

- Split multibit inputs into individual bits or ranges of bits


FPGA supported:	Supported
Facing	→ East
Fan Out	16
Bit Width In	16
Appearance	Centered
Spacing	1
Bit 0	0 (1 Top)
Bit 1	1
Bit 2	2
Bit 3	3
Bit 4	4
Bit 5	5
Bit 6	6
Bit 7	7
Bit 8	8
Bit 9	9
Bit 10	10
Bit 11	11
Bit 12	12
Bit 13	13
Bit 14	14
Bit 15	15

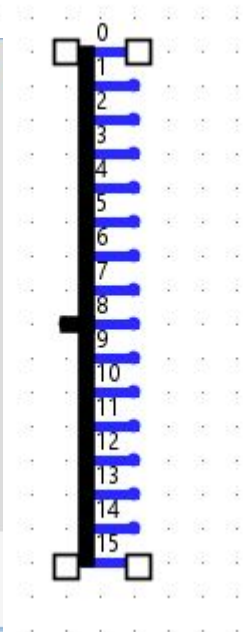

Bit Extenders

- Extends the input bit to chosen output bit width
- Choose extension types like signed or zero extended

Bit Extender (470,430)	
FPGA supported:	Supported
Bit Width In	8
Bit Width Out	16
Extension Type	Sign

 

Constants


- Constant values, useful for comparators

Constant (300,500)		
	FPGA supported:	Supported
Facing		→ East
Data Bits		8
Value		0xff



Comparators

 - Compares two different values in either unsigned or two's complement



Comparator (630,480)

FPGA supported:	Supported
Data Bits	8
Numeric Type	2's Complement




Control Review

- The “brain” of the datapath
- Decodes the instruction and provides selectors(PCSel, ImmSel, BrUn) to the rest of the datapath elements



 
2.1 c)

- PCSel:
 - 0 corresponds with PC+4 (no branch)
 - 1 corresponds with ALU (PC + IMM)
 - For branching instructions, PCSel is known after EX




2.1 c)

- ImmSel:
 - ImmSel can be I, B, S, J, U

 

 
2.1 c)

- BrUn, BrEq, BrLt:
 - Control outputs BrUn to branch comp
 - Branch comp returns BrEq and BrLT according to BrUn
 - BrUn is only 1 for unsigned branch instructions



 2.1 c)


- BSel, ASel:
 - 1 for ASel corresponds to PC, 0 corresponds to rs1
 - 1 for BSel corresponds to Imm, 0 corresponds to rs2
- ALUSel:
 - Chooses which operation
 - 16 different values, corresponding to operations like add, ori, etc.





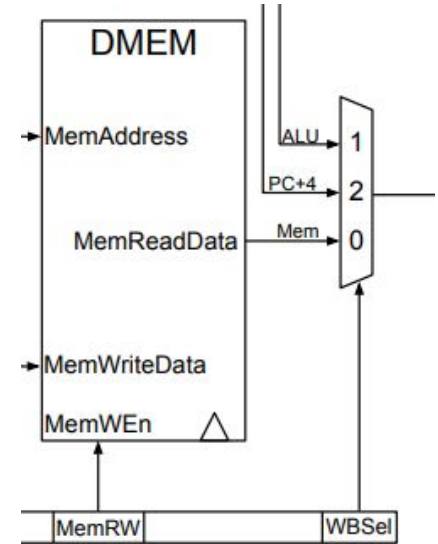2.1 c)

- MemRW:
 - Value of 1 allows for writes to memory, and vice versa for 0
- WBSel:
 - Chooses which value gets passed to regfile to be saved



Timing Review

- We go from state element to state element (register to register)

$$t_{clk-to-q} + t_{logic,Max} + t_{setup} \leq t_{clk-period}$$

$$t_{clk-to-q} + t_{logic,Min} \geq t_{hold}$$



Pipelining

- Maximizes efficiency by allowing for higher clock frequency
- To pipeline, we put registers between stages to hold intermediate values
- To consider timing when it comes to pipelined circuits, consider the delay of each stage and clock period will be determined by the stage with max delay