

# CS61C: Great Ideas in Computer Architecture (aka Machine Structures)

## Lecture 11: FSMs, Synchronous Digital Systems

Instructors: Rosalie Fang, **Charles Hong**, Jero Wang


# Announcements

- Labs 3 and 4 due today 7/11
- Homework 3 due tomorrow (Wednesday 7/12)
- Midterm review sessions:
  - Today, 5-7pm in the Woz (Soda 430)
  - Thursday, 3-5pm in Cory 540AB

# Last Time: Combinational Logic


- Logic gates can be built out of transistors
- More complicated circuits can be built out of logic gates
- Logic gates and circuits can be represented with:
  - Circuit diagrams
  - Truth tables
  - Boolean algebra expressions
- Manipulating Boolean algebra expressions
  - Laws of Boolean algebra
  - Sum-of-products representation
- Applications of circuits
  - Arithmetic logic unit (ALU)
- Next: How do we store values in circuits?

# CS 61C Hardware Roadmap

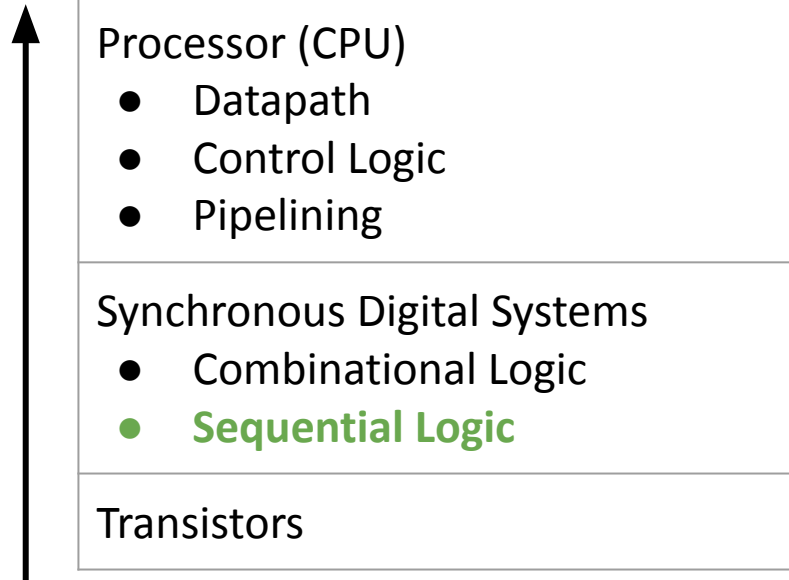


# Waveforms

- Graph of a signal's value over time

 

For 1-bit signals, high=1, low=0.

 


Grayed out = unknown or garbage value.


For  $n$ -bit signals, we can write the value on the waveform.

# Waveforms

- Graph of a signal's value over time

 

An ideal signal looks like this, but...

 


...in reality, signals are noisy!

# Finite State Machines (FSMs)
 
# Motivating FSMs

- We can AND signals together
- What if we want to AND three time steps, of one signal?
  - Set an output to 1, if input was 1 for the last three time steps






# Finite State Machines (FSMs)

- An FSM consists of:
  - A set of states
  - A transition function:  $f(\text{current state, input}) \rightarrow \text{next state, output}$
- To run an FSM, repeat these steps:
  - Receive an input
  - Based on current state and input, move to the next state and generate an output


 
# FSM: State Transition Diagram

- S0, S1, S2 are the states
- Each arrow represents a transition
  - Arrow from current state to next state
  - Left label on arrow is the input
  - Right label on arrow is the output
- Example of arrow transition:
  - Arrow from S0 to S1, labeled 1/0
  - If you're at state S0 and receive input 1, then move to state S1, and output 0
- Example of arrow transition:
  - Arrow from S2 to S0, labeled 1/1
  - If you're at state S2 and receive input 1, then move to state S0, and output 1



 
 
# FSM: Waveform

Given this state transition diagram and input signal, what is the output signal?



  
# FSM: Waveform

What pattern in the input is this FSM detecting?


 
# FSM: Transition Function Circuit

- Transition function is combinational logic with:
  - Two inputs: current state (CS) and input (in)
  - Two outputs: next state (NS) and output (out)
  - Each state is labeled with a unique binary number




You can also derive a circuit and Boolean algebra expression for the other two outputs, NS0 and NS1.

CS	in	NS	out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

$$\text{out} = (\text{CS1})(\neg\text{CS0})(\text{in})$$
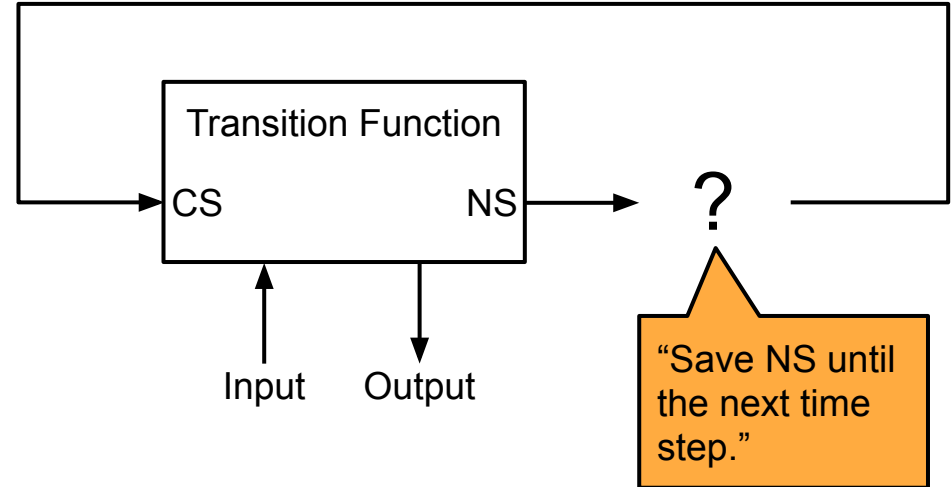
# FSM: State

How do we differentiate  
between timesteps?  
How do we “save” which  
state we’re in?



# Sequential Logic: Clock and Registers


# Synchronous Digital Systems

- What does it mean?
- Synchronous: behaves in time with each other, at the same time, simultaneously
- Digital: with regards to signals, takes on only discrete values
  - Different from analogue which takes on intermediate values
- Systems: a group of interdependent elements that form a whole
- Synchronous Digital System: elements that behave in time with one another as part of a greater whole, producing discrete signal outputs



 
# Clock

- Clock: Signal that alternates between 0 and 1
- Rising edge: Time when the clock switches from 0 to 1
- Falling edge: Time when the clock switches from 1 to 0
- Clock period: Time between rising edges
- Clock frequency: Number of rising edges per second
  - Frequency =  $1 / \text{period}$



 
# Flip-Flop


- Inputs:
  - One-bit value D
  - One-bit clock value (often drawn as triangle)
- Outputs:
  - One-bit value Q
- Behavior:
  - On the rising edge of the clock, set  $Q=D$
  - At all other times, do nothing
- Usage:
  - Store data: Between rising edges, the output value at Q will stay steady
  - Control the flow of data: Hold data at the D input until the next rising edge



# Flip-Flop Timing Example

 


# Flip-Flop Timing Example

 

 
# Registers

- *n*-bit register: *n* flip-flops bundled together
  - Each flip-flop stores 1 bit of data
  - The register stores *n* bits of data in total
- Inputs:
  - *n*-bit value D
  - One-bit clock value
- Outputs:
  - *n*-bit value Q
- Behavior:
  - On the rising edge of the clock, set  $Q=D$
  - At all other times, do nothing



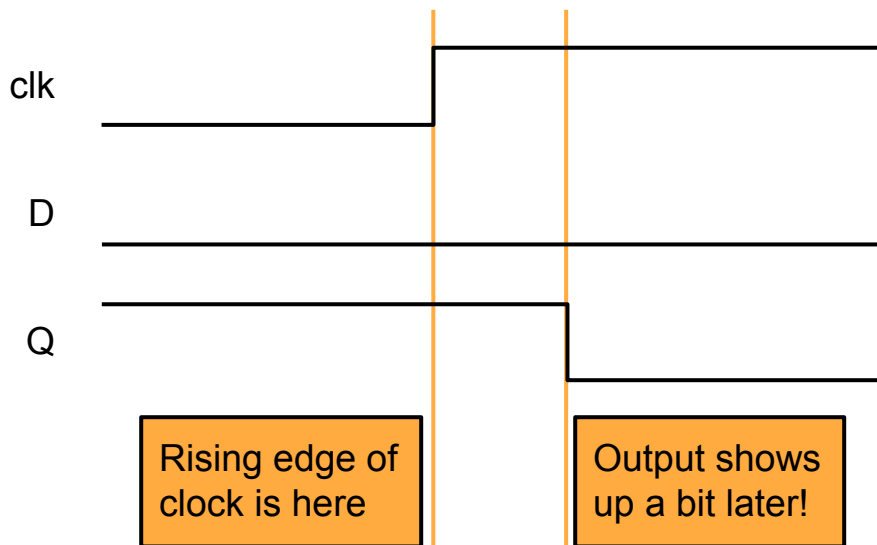
# Register Delay: clk-to-q delay


- Registers can't transfer the D input to Q output instantly
- clk-to-q delay: Time it takes after the rising edge for the Q output to change


 
## Flip-Flop Timing with 1 ns clk-to-q Delay


 
# Flip-Flop Timing with 1 ns clk-to-q Delay






# Combinational Delay
 
# Combinational Delay



- Combinational logic circuits have propagation delay: time it takes for the output to change after the input changes
- Example: Adder circuit that sets  $\text{Out} = A + B$ :



 
 
# Why does combinational delay exist?

- Transistors are not perfect switches.
- If electrons are water molecules, transistor resistance like pipe diameters, and capacitors are buckets.

An “on” p-type transistor **fills up** the output capacitor with charge.



  An “on” n-type transistor **drains** the bucket.







# Why does combinational delay exist?

- Transistors are not perfect switches.
- If electrons are water molecules, transistor resistance like pipe diameters, and capacitors are buckets.


Side note: Filling and draining the “bucket” uses energy!

    The main reason why your devices heat up when they’re working hard.




# Combinational Delay

 - Example
  - OR gates have a delay of 5 ps
  - Suppose A, B, C change at  $t=0$  ps. When does the output change?
  - Wait 5 ps for  $A + B$  to be calculated
  - Then wait 5 ps for  $(A + B) + C$  to be calculated
- We have to consider the **critical path**: the path between input and output with the longest delay


 
# Three-way OR with registers

- Delay assumptions:
  - OR gate delay = 5 ps
  - clk-to-q delay = 3 ps
  - clock period = 20 ps
- Timing:
  - $t=0\text{ps}$ : Rising edge of clock
  - $t=3\text{ps}$ : Inputs appear at Q output of the left-side registers
  - $t=13\text{ps}$ : Output appears at D input of the right-side register
  - $t=20\text{ps}$ : Rising edge of clock
  - $t=23\text{ps}$ : Output appears at Q output of the right-side register




# Maximizing Clock Frequency

- Problem

- Computation was done at  $t=13\text{ps}$
- But we had to wait until the next rising edge ( $t=20\text{ps}$ ), plus the clk-to-q delay ( $t=23\text{ps}$ ), to access the result

- Solution: Reduce the time between rising edges

 
- Shorter clock period, higher clock frequency
- More computations per second


 
# Maximizing Clock Frequency

- Can we increase clock frequency as much as we want?


- Suppose we set the clock period to be 10 ps
- Problem: Computation isn't finished on the next rising edge of the clock!
- What is the maximum clock frequency that produces correct behavior?
- Is it safe to have the rising edge at 13 ps, exactly when the computation is done?




 
# Register Constraints: Setup Time


- Intuition:
  - Assume clock period = 20ps
  - What if signal arrives at the D input of the right-side register at 19.9ps?
  - At the rising edge ( $t=20\text{ps}$ ), the D input hasn't stabilized yet. Register doesn't know what to send to the Q output!
- Setup time: Time before rising edge when the D input must be stable



D input cannot change after this, so the register can read a stable value.

 
# Register Constraints: Hold Time

- Intuition:
  - Assume clock period = 20ps
  - What if a new signal arrives at the D input of the right-side register at 20.1ps?
  - After the rising edge ( $t=20\text{ps}$ ), the D input isn't stable. Register doesn't know what to send to the Q output!
- Setup time: Time after rising edge when the D input must be stable



D input cannot change before this, so the register can read a stable value.

# Setup and Hold Time Violations

 

# Maximizing Clock Frequency

- Setup time and combinational delay constraint:

**Clock period  $\geq$  clk-to-q delay + longest combinational delay + setup time**


- After the rising edge, we have to wait clk-to-q delay for the Q output to change
- Then, we have to wait the longest combinational delay for the result to appear at the D input
- Then, we have to hold that D input stable for the setup time

# Satisfying Hold Time Constraints

- Hold time constraint:


$$\text{Hold time} \leq \text{clk-to-q delay} + \text{shortest combinational delay}$$

 - After the rising edge, we have to wait clk-to-q delay for the Q output to change
  - Then, after the shortest combinational delay, one of the D inputs will change
  - We need the hold time to be over by the time the D input changes
- What happens if you connect two registers in a row?



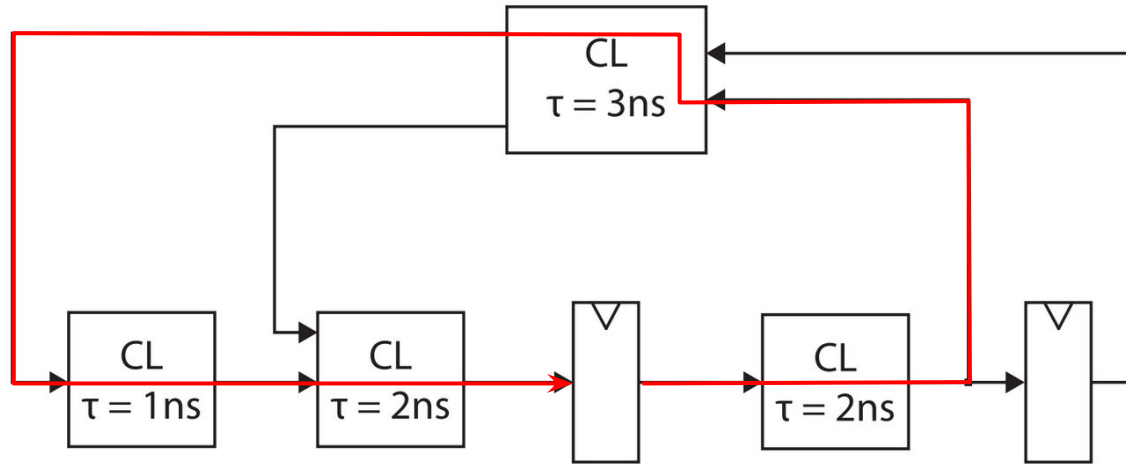
# Finding Critical Paths

- **Critical path** can also be thought of as the “longest path between registers”
- To find: check all paths between two registers, or a register and itself



# Memory
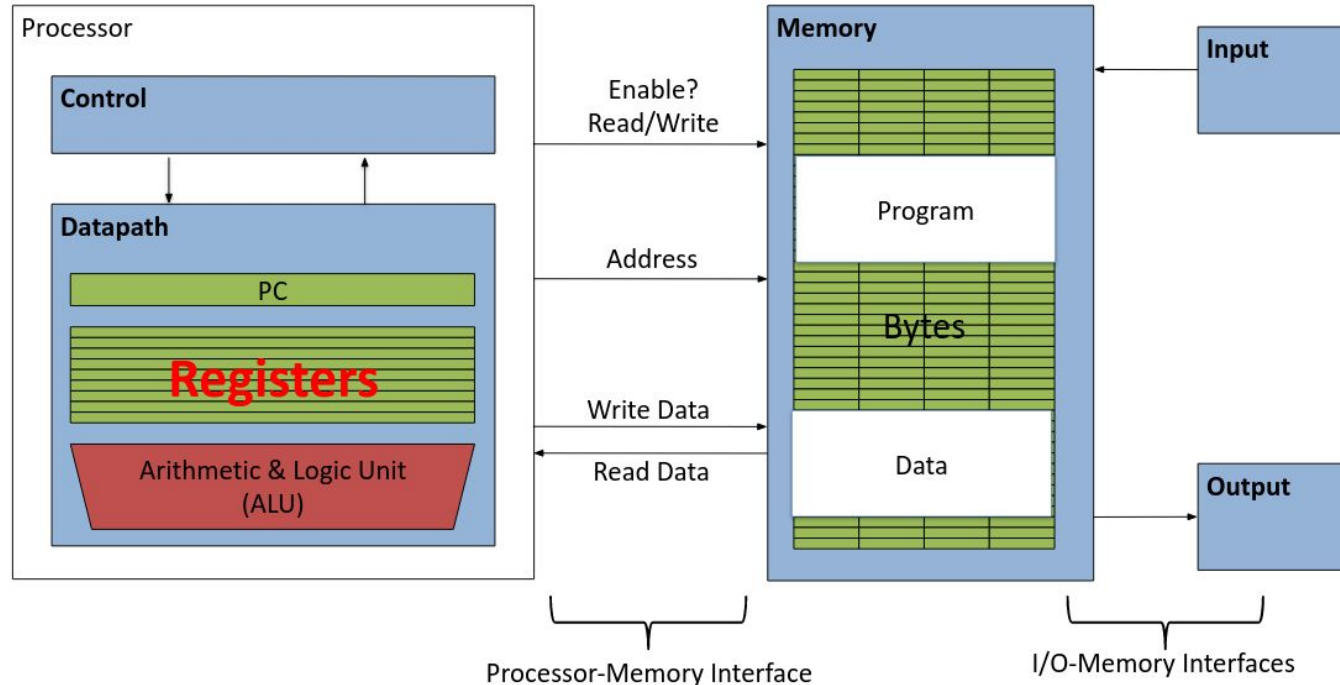
# Recall: Registers are Inside the Processor (Memory is Not!)





# Memory vs. Registers

- Memory is different from registers
  - Memory is in a different location on hardware
  - We don't have space for  $2^{32}$  registers on the processor!
- The memory unit is abstracted away for this class
  - Memory accesses are usually much slower than register accesses, but for now we'll assume they're about as fast as register accesses
  - In a couple weeks, we'll see how we can achieve this with caches

# Summary, Next Time (1/2)

- Finite State Machines (FSMs)
  - Set of states, with a transition function:  $f(\text{current state, input}) \rightarrow \text{next state, output}$
  - In a circuit: Transition function is combinational logic, current state stored in a register
- Sequential logic blocks
  - Waveforms show how signals change over time
  - Clock: Signal that alternates between 1 and 0. Rising edge used for timing a circuit.
  - Flip-flop: On the rising edge of the clock, set Q output = D input
  - Register:  $n$  flip-flops bundled together. Used to store values in the circuit and control signal flow.
- Register delays
  - clk-to-q delay: Time after the rising edge when Q output is updated with D input
  - Setup time: Time before the rising edge when the D input must be stable
  - Hold time: Time after the rising edge when the D input must be stable

## Summary, Next Time (2/2)

- Combinational logic circuits have propagation delay
  - Calculate delay by looking for the critical path (longest path through the circuit)
- Memory
  - Interface between processor and memory for writing to and reading from memory addresses
- Next time: Use combinational and sequential logic blocks to build a circuit that runs RISC-V instructions (also known as: CPU)!